

数字电路作业

Verilog编程-Homework

姜俊彦 2022K8009970011 本科部

编程题 1: 用Verilog HDL编写一个4路随机仲裁器。

编程题1源码: (四路随机仲裁器)

```
module random_Arb4 #(parameter N=4)
(
    input clk,rstn,
    input [N-1:0] req_i,
    output [N-1:0] ack_i,
    output req_o,
    input ack_o
);
    genvar i;
    wire [N-1:0] prio;
    wire [N-1:0] q;
    assign req_o = |req_i;

    lfsrN #(N)random (.clk(clk),.rstn(rstn),.q(q));
    transfrom transfrom(.q(q),.prio(prio));

    reg [N-1:0] ack_i_reg;

    generate
        for (i = 0; i<N; i=i+1) begin
            if(i==0)begin
                assign ack_i[0]=prio[0]&req_i[0]&ack_o;
            end
            else begin
                assign ack_i[i]=prio[i]&req_i[i]&ack_o;
            end
        end
    endgenerate
endmodule //5B-13_ArbPriority_noroute

module lfsrN #(parameter N=4)(
    input clk,rstn,
    output [N-1:0] q
);
    reg [N-1:0] q;
    always @(posedge clk or negedge rstn) begin
        if(!rstn) begin
            q<=4;
        end
        else begin
```

```
            q[N-1:1]<=q[N-2:0];
            if(N==3) q[0]<=q[2]^q[1];
            if(N==4) q[0]<=q[3]^q[2];
            if(N==5) q[0]<=q[4]^q[2];
            if(N==6) q[0]<=q[5]^q[4];
            if(N==7) q[0]<=q[6]^q[5];
            if(N==8) q[0]<=q[7]^q[5]^q[4]^q[3];
        end
    end
endmodule

module transfrom
(
    input [3:0] q,
    output [3:0] prio
);
    reg [3:0]prio_reg;
    always @(q) begin
        if(q>=1&q<=3) begin
            prio_reg=4'b0001;
        end
        else if(q>=5&q<=7) begin
            prio_reg=4'b0010;
        end
        else if(q>=9&q<=11) begin
            prio_reg=4'b0100;
        end
        else if(q>=13&q<=15) begin
            prio_reg=4'b1000;
        end
        else begin
            prio_reg=4'b0000;
        end
    end
    assign prio=prio_reg;
endmodule
```

编程题1源码 (四路动态随机优先级仲裁器)

```
module randomprio_Arb4 #(parameter N=4)
(
    input clk,rstn,
    input [N-1:0] req_i,
    output [N-1:0] ack_i,
    output req_o,
    input ack_o
);
    genvar i;
    wire token[2*N-1:0];
    wire [N-1:0] prio;
    wire [N-1:0] q;
    assign req_o = |req_i;

    lfsrN #(N)random (.clk(clk),.rstn(rstn),.q(q));
```

```

transfrom transfrom(.q(q),.prio(prio));

reg [N-1:0] ack_i_reg;

generate
  for (i = 0; i<N; i=i+1) begin
    if(i==0)begin
      assign ack_i[0]=(token[N-1]|prio[0])&req_i[0]&ack_o;
      assign token[0]=(token[N-1]|prio[0])&~req_i[0];
      assign token[N]=token[N-1]&~req_i[0];
    end
    else begin
      assign ack_i[i]=(token[i-1]|prio[i]|token[N+i-1])&req_i[i]&ack_o;
      assign token[i]=(token[i]|prio[i])&~req_i[i];
      assign token[N+i]=token[N+i-1]&~req_i[i];
    end
  end
endgenerate
endmodule //5B-13_ArbPriority_noroute

```

```

module lfsrN #(parameter N=4)(
  input clk,rstn,
  output [N-1:0] q
);
  reg [N-1:0] q;
  always @(posedge clk or negedge rstn) begin
    if(!rstn) begin
      q<=4;
    end
    else begin
      q[N-1:1]<=q[N-2:0];
      if(N==3) q[0]<=q[2]^q[1];
      if(N==4) q[0]<=q[3]^q[2];
      if(N==5) q[0]<=q[4]^q[2];
      if(N==6) q[0]<=q[5]^q[4];
      if(N==7) q[0]<=q[6]^q[5];
      if(N==8) q[0]<=q[7]^q[5]^q[4]^q[3];
    end
  end
endmodule

```

```

module transfrom
(
  input [3:0] q,
  output [3:0] prio
);
  reg [3:0]prio_reg;
  always @(q) begin
    if(q>=1&q<=3) begin
      prio_reg=4'b0001;
    end
    else if(q>=5&q<=7) begin

```

```

      prio_reg=4'b0010;
    end
    else if(q>=9&q<=11) begin
      prio_reg=4'b0100;
    end
    else if(q>=13&q<=15) begin
      prio_reg=4'b1000;
    end
    else begin
      prio_reg=4'b0000;
    end
  end
  assign prio=prio_reg;
endmodule

```

编程题1测试模块源码:

```

`timescale 1ns/1ps

module test;
  reg clk,rstn;
  reg [3:0] req_i;
  reg ack_o;
  wire [3:0] ack_i;
  wire req_o;

  random_Arb4 #(4)
  dut(.clk(clk),.rstn(rstn),.req_i(req_i),.ack_i(ack_i),.req_o(req_o),.ack_o(ack_o));
  //randomprio_Arb4 #(4)
  dut(.clk(clk),.rstn(rstn),.req_i(req_i),.ack_i(ack_i),.req_o(req_o),.ack_o(ack_o));

  initial begin
    clk=0;
    forever begin
      #5 clk=~clk;
    end
  end
  initial begin
    req_i<=0;
    ack_o=1;
    #2000
    ack_o=0;
    #100
    ack_o=1;
  end
  initial begin
    rstn<=1;
    #3 rstn<=0;
    #13 rstn<=1;
  end
end

```

```

always @(posedge clk) begin
    if(~req_i[0]) begin
        req_i[0] <= $random;
    end
    if(~req_i[1]) begin
        req_i[1] <= $random;
    end
    if(~req_i[2]) begin
        req_i[2] <= $random;
    end
    if(~req_i[3]) begin
        req_i[3] <= $random;
    end
end

```

```

always @(negedge clk) begin
    if(ack_i[0])begin
        req_i[0] <= 0;
    end
    if(ack_i[1])begin
        req_i[1] <= 0;
    end
    if(ack_i[2])begin
        req_i[2] <= 0;
    end
    if(ack_i[3])begin
        req_i[3] <= 0;
    end
end

```

```

integer n0=0,n1=0,n2=0,n3=0;
always @(negedge clk) begin
    if(ack_i[0]) begin
        n0=n0+1;
    end
    if(ack_i[1]) begin
        n1=n1+1;
    end
    if(ack_i[2]) begin
        n2=n2+1;
    end
    if(ack_i[3]) begin
        n3=n3+1;
    end
end

initial begin
    $dumpfile("random_Arb4_test.vcd");
    $dumpvars(0);
    #400000

```

```

        $display($stime, ": port 0 is answered %d times.\n",n0);
        $display($stime, ": port 1 is answered %d times.\n",n1);
        $display($stime, ": port 2 is answered %d times.\n",n2);
        $display($stime, ": port 3 is answered %d times.\n",n3);
        $finish();
    end

endmodule

```

编程题1仿真结果:

```

20149@Jiuhao-S-System-Center MINGW64 ~/Verilog-demo
$ vvp random_Arb4
VCD info: dumpfile random_Arb4_test.vcd opened for output.
4000000: port 0 is answered      63194 times.

4000000: port 1 is answered      69768 times.

4000000: port 2 is answered      71475 times.

4000000: port 3 is answered      65773 times.

20149@Jiuhao-S-System-Center MINGW64 ~/Verilog-demo
$ iverilog -o randomprio_Arb4 -s test src/randomprio_Arb4.v test/randomprio_Arb4_test.v
20149@Jiuhao-S-System-Center MINGW64 ~/Verilog-demo
$ vvp randomprio_Arb4
VCD info: dumpfile randomprio_Arb4_test.vcd opened for output.
400000: port 0 is answered      10965 times.

400000: port 1 is answered      9652 times.

400000: port 2 is answered      10041 times.

400000: port 3 is answered      9920 times.

```

编程题 2: 用Verilog HDL编写一个输出为寄存器直接输出的FIFO缓冲, 缓冲深度为8, 数据宽度为4位。

编程题2源代码

```

module fifo_register_out #(parameter dw=4,L=8)
(
    input clk,rstn,
    input [dw-1:0] d_in,
    input req_in,
    output ack_in,
    output [dw-1:0] d_out,
    output req_out,
    input ack_out
);
    reg [dw-1:0] data [L-1:0];
    reg [L-1:0] wp;
    reg [dw-1:0]out;

    assign req_out=|wp;
    assign ack_in=(wp==L)?0:1;
    assign d_out=out;

```

```

always @(posedge clk or negedge rstn) begin
    if(!rstn) begin
        wp<=0;
    end
    else begin
        if(req_in&ack_in&(~(req_out&ack_out))) begin
            wp<=(wp==L)?L:wp+1;
            data[wp]<=d_in;
        end
        else if(req_out&ack_out&(~(req_in&ack_in))) begin
            wp<=(wp==0)?0:wp-1;
            data[3]<=0;
            data[2]<=data[3];
            data[1]<=data[2];
            data[0]<=data[1];
            out<=data[0];
        end
        else if(req_in&ack_in&req_out&ack_out)begin
            data[2]<=data[3];
            data[1]<=data[2];
            data[0]<=data[1];
            out<=data[0];
            data[wp-1]<=d_in;
        end
        else begin
            ;
        end
    end
end
endmodule

```

//深度为L的FIFO缓冲

编程题2测试代码

```

`timescale 1ns/1ps
module test;
    parameter dw=4,L=8;
    reg clk,rstn;
    reg [dw-1:0] d_in;
    reg req_in;
    wire ack_in;
    wire [dw-1:0] d_out;
    wire req_out;
    reg ack_out;

    reg [dw-1:0] localfifo[L-1:0];
    integer wp=0;
    integer data_num=0;
    integer full_num=0;
    integer empty_num=0;

```

```

    fifo_register_out #(dw,L)
    dut(clk,rstn,d_in,req_in,ack_in,d_out,req_out,ack_out);

    initial begin
        clk=0;
        forever begin
            #5 clk=~clk;
        end
    end


    initial begin
        rstn=1;
        #3 rstn=0;
        #13 rstn=1;
    end

    always @(posedge clk) begin
        req_in<=$random;
        d_in<=$random;
        ack_out<=$random;
    end

    initial begin
        $dumpfile("fifo_register_out.vcd");
        $dumpvars(0);
        #10000 $finish();
    end
endmodule

```

编程题2仿真波形

 

编程题3: 用Verilog HDL编写一个交通灯, 按照红灯10个时钟周期, 黄灯1个时钟周期, 绿灯9个时钟周期, 黄灯2个时钟周期的顺序循环。

编程题3源码

```

module traffic_light
(
    input clk,rstn,
    output [1:0]signal //2'b00: Error, 2'b01:red, 2'b10:green, 2'b11:yellow
);
    reg [4:0] cnt;
    reg [1:0] signal_reg;

    always @(posedge clk or negedge rstn) begin
        if(!rstn) begin
            cnt<=22;

```

```

        end
    else if(cnt <21) begin
        cnt<=cnt+5'b00001;
    end
    else begin
        cnt<=5'b00000;
    end
end

always @(cnt) begin
    if(cnt<10) begin
        signal_reg=2'b01;
    end
    else if(cnt<11) begin
        signal_reg=2'b11;
    end
    else if(cnt<20) begin
        signal_reg=2'b10;
    end
    else if(cnt<22) begin
        signal_reg=2'b11;
    end
    else begin
        signal_reg=2'b00; //Error Signal
    end
end

assign signal=signal_reg;
endmodule

```

编程题3测试代码

```

`timescale 1ns/1ps

module test;
    reg clk;
    reg rstn;
    wire [1:0]signal;

    traffic_light dut(.clk(clk),.rstn(rstn),.signal(signal));

    initial begin
        clk=0;
        forever begin
            #5 clk=~clk;
        end
    end

    initial begin
        rstn=1;
        #3
        rstn=0;
        #13 rstn=1;
    end
end

```

```

    initial begin
        $dumpfile("traffic_light_test.vcd");
        $dumpvars(0);
        #300 $finish();
    end
endmodule

```

编程题3仿真波形

